

POWER SYSTEM -II
LAB MANUAL
(EE-328)
VI SEMESTER
ELECTRICAL ENGINEERING



RAO PAHLAD SINGH GROUP OF INSTITUTIONS
BALANA (MOHINDER GARH) 123029
(DEPARTMENT OF ELECTRICAL ENGINEERING)

Submitted by:
Karambir Sheoran
Asstt.Professor ,EE Deptt.


LIST OF EXPERIMENTS

Sr. No.	TITLE	Page No.
1.	To study the performance of under voltage relay.	3
2.	To study performance characteristics of typical DC distribution system in radial Configuration.	4
3.	To study performance characteristics of typical DC distribution system in ring main configuration.	6
4.	Testing of breakdown strength of a transformer oil.	8
5.	To study characteristics of MCB & HRC Fuse.	10
6.	To study the performance of an over voltage relay.	12
7.	Determine the ABCD,H, Z and Image parameters of Short Transmission Line	13
8.	Determine the ABCD,H,Z and Image parameters of Medium Transmission Line	16
9.	Determine the ABCD,H,Z and Image parameters of Long Transmission Line	19
10.	To study flash point test of transformer oil.	22

EXPERIMENT NO. - 1

AIM: - To study the performance of under voltage relay.

Circuit Diagram:-

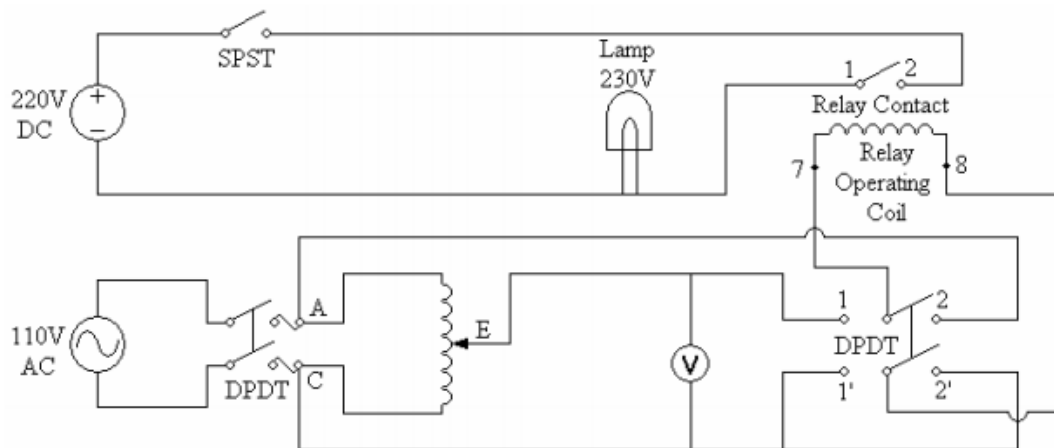**Theory:**

The operating torque is provided by the spring and restraining torque is proportional to the Voltage. $K_1 - K_2V^2 > 0$

Procedure:

- Chose the required relay setting (% of 110V) and TSM
- By the Autotransformer set the circuit to a particular PSM with DPDT at 1
- Put the DPDT to 2 to reset the Relay (disc should return to its original position)
- Switch over to 1 (DPDT), record the time of operation of the Relay, till the contactor trips.
- Repeat 1-4 for at least two TSMs and two relay settings.

Precaution:

- Slowly increase the Voltage to the required value.

EXPERIMENT NO. -2

AIM: - To study performance characteristics of typical DC distribution system in radial.

Requirements:-

- Main Cord
- Patch Cords
- 40W bulbs (5)

Theory:

Whole of the power system can be subdivided in to number of radial feeders fed from one End. Generally such radial feeders are protected by over current and earth fault relays Used as primary relays for 11 kV and 66 kV lines. For lines of voltage rating beyond 66 KV, distance protection is applied as a primary protection whereas over current and earth Fault relays are used as back up relays.

A simplified radial feeder network without transformers (in actual practice transformers Do exist at substations) is shown in single line diagram of fig. 1.1 below.

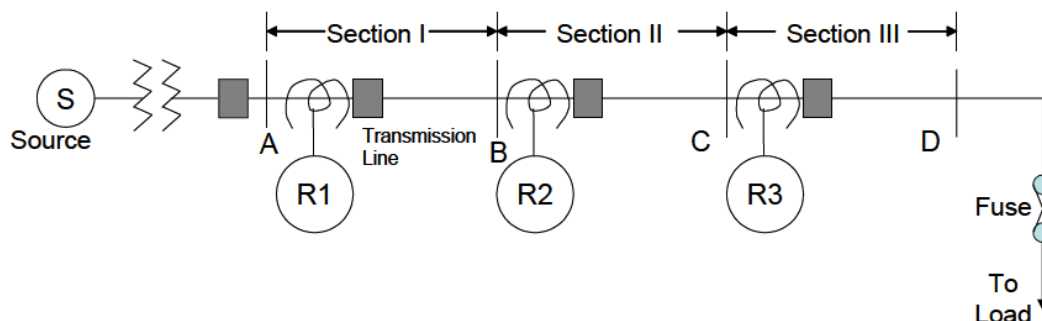


Fig. 1.1. A Typical Radial Transmission Line

If the fault occurs in distribution network, fuse should isolate the faulty section. Should The fuse fail, relay R3 shall give back-up protection. Relays R1, R2, and R3 act as primary Relays for faults in section I, section I, and section III respectively. If fault in section III is Not cleared by relaying scheme at relaying point R3, relay R2 will act as a back-up. Similarly back-up protection is provided by relay R1 for faults in section II. A, B, C and D Are substations in fig. 1.1 .

Procedure:

1. First of all make sure that the earthing of your laboratory is proper and connected to the Terminal provided on back side of the panel.
2. Make sure that the variac knob is at zero position.
3. Make the connection according to Diagram.
4. Now insert 40W bulbs into bulb holders.
5. Now switch ON the AC mains and MCB of your trainer.
6. Now vary the knob of variac up to 220V.
7. Switch ON all the toggle switches S1, S2, S3, S4 and S5. (Upward direction).
8. You will observe all the bulbs in Radial Distribution section will glow. That means all the Connections are right.
9. Now put the variac knob at zero position.
10. Connect voltmeter terminal V4 to – ve terminal of Consumer4.
11. Now insert one end of patch cord to V3 terminal & second end will connect to measured terminals.
12. Once again vary the knob of variac up to 220V.
13. Now observe the voltage drop in each Consumer terminal and note the readings.
14. Put the variac knob at zero position.
15. Switch Off the mains and remove all the connection and bulbs.

Results:

If the distributor is connected to the supply system on one end only then the end of the feeder Nearest to the generating station would be heavily loaded and the Consumers at the distance end of the distributor would be subjected to large voltage variations as the load varies.

EXPERIMENT NO. -3


AIM: - To study performance characteristics of typical DC distribution system in ring.

Requirements:-

- Main Cord
- Patch Cords
- 40W bulbs (5)

Theory:

One ring network of distributors is fed by more than one feeder. In this case if one feeder is under fault or maintenance, the ring distributor is still energized by other feeders connected to it. In this way the supply to the consumers is not affected even when any feeder becomes out of service. In addition to that the ring main system is also provided with different section Isolates at different suitable points. If any fault occurs on any section, of the ring, this section can easily be isolated by opening the associated section isolators on both sides of the faulty Zone.

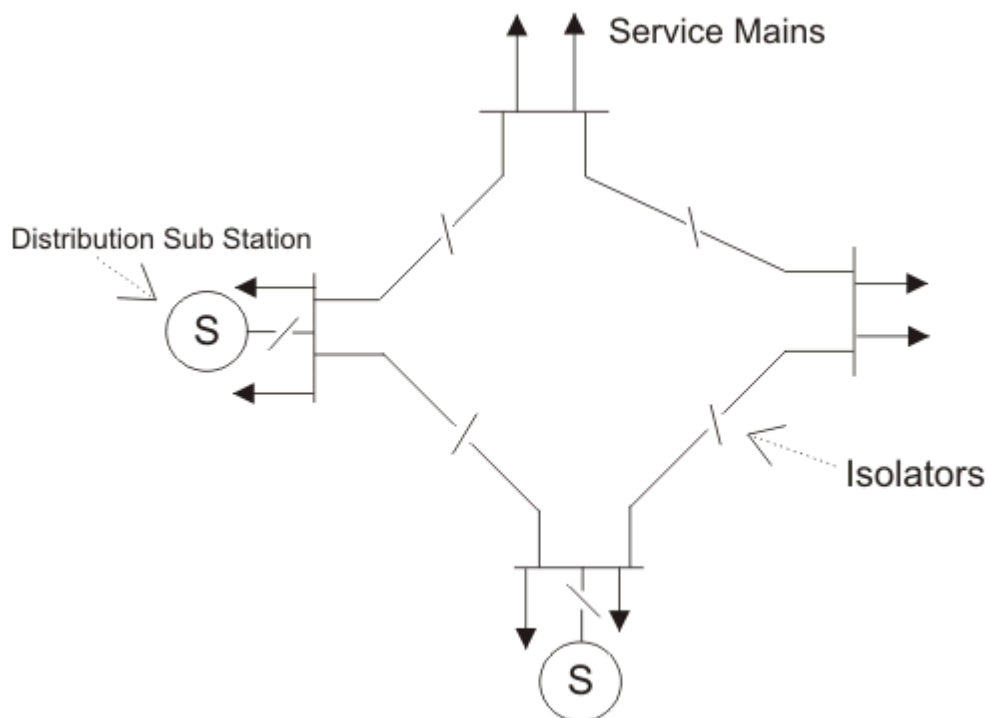

Procedure:

- First of all make sure that the earthing of your laboratory is proper and connected to the Terminal provided on back side of the panel.
- Make sure that the variac knob is at zero position.
- Make the connection according to Diagram.
- Now insert 40W bulbs into bulb holders.
- Now switch ON the AC mains and MCB of your trainer.
- Now vary the knob of variac up to 220V.
- Switch ON all the toggle switches S1, S2, S3, S4 and S5. (Upward direction).
- You will observe all the bulbs in Radial Distribution section will glow. That means all the Connections are right.
- Now put the variac knob at zero position.
- Connect voltmeter terminal V6 to –ve terminal of source 1.
- Now insert one end of patch cord to V5 terminal & second end will connect to measure Terminals.
- Once again vary the knob of variac up to 220V.
- Now observe the voltage drop in each Consumer terminal and note the readings.
- Put the variac knob at zero position.
- Switch Off the mains and remove all the connection and bulbs.

Result:

If the distributor is connected to the supply system at both ends then the load is equally distributed at both ends and no voltage variations as the load varies.

EXPERIMENT NO. - 4

AIM: -Testing of breakdown strength of transformer oil.

Requirements:-

1. Transformer oil test kit
2. Transformer oil.

Theory:-

The insulation oil of voltage- and current-transformers fulfills the purpose of insulating as well as Cooling. Thus, the dielectric quality of transformer oil is a matter of secure operation of a transformer. As transformer oil deteriorates through aging and moisture ingress, transformer oil should, depending on economics, transformer duty and other factors, be tested periodically.

Procedure:-

- Make sure that the mains switch of control panel is off position.
- Now take out the acrylic oil cup from the setup.
- Adjust the gap in between both electrodes in the oil cup with the help of “GO” and “NOGO” gauge provided
- Fill the transformer oil in the acrylic oil cup up to top level and keep the oil cup on the aluminum studs carefully placed on output insulators.
- Let the oil settle for half minute.
- Cover the oil cup & closed acrylic top door of the control panel properly.
- Connect the main cord to the mains socket (230V).
- Switch ON mains supply as well as mains switch provide in front panel of control setup.
- After switch on the panel, green neon lamp will glow.it indicate that input supply appears at the control setup but high voltage is off.

- If green lamp does not glow, then check whether acrylic door is properly closed or not.
- Now turn the toggle switch at 'Raise' position.
- After that turn on the HV On switch on the panel then Red neon lamp will glow. It indicate that high voltage is being generated at the secondary winding of the transformer that is high Voltage is present between the electrodes in the oil cup.
- At some point of voltage, the insulation of the test oil get breakdown and a spark is seen in between the electrodes instantaneously.
- Record the reading of voltmeter into observation table.
- Repeat the above steps and take no. of readings in fixed time interval.
- Switch off the main supply.

Results:-

We have successfully tested breakdown strength of a transformer oil.

EXPERIMENT NO. - 5


AIM: - To study characteristics of MCB & HRC Fuse.

Requirements:-

- Rheostat 220 ohm.2.8 A
- Connecting leads

Theory :-

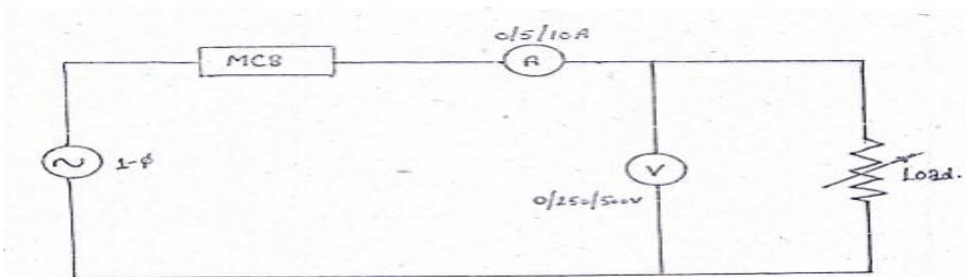A current limiting protective device cuts off a short circuit in less than one half cycle and that too before it reaches its total prospective highly destructive value fuses are current limiting time . By maintaining a minimum ratio of fuse – ampere rating between upstream and downstream fuse selective coordination is assured which prevents the power failure caused over current conditions .



Procedure:-

- Make sure that the switch S1 is off means the circuit is open.
- Make the connection according to the diagram.
- Put the B type MCB knob upwards.
- Switch On the mains, LCD switch S2 and S1 switch.
- With the help of variac and rheostat adjust the current say 9A.
- After adjusting the current switch off S1.
- Now again on the switch S1 and measure the current reading.
- Now switch off the switch S1 & then switch S2.
- Repeat the process and take 5-6 readings on the current rating.

- Switch off the mains supply.


Results:-

We have successfully studied about the MCB and HRC fuse.

EXPERIMENT NO. -6

AIM: -To study the performance of over voltage relay.

Circuit Diagram:-

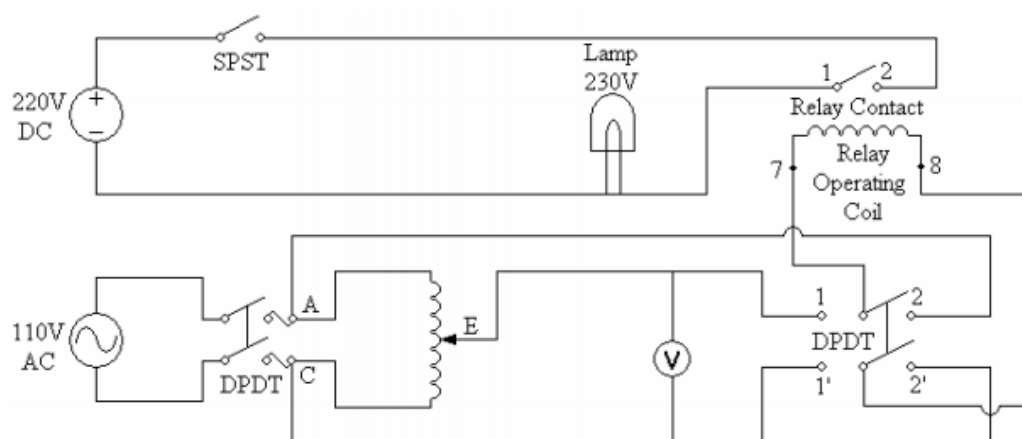

Theory:

The operating torque is provided by the spring and restraining torque is proportional to the voltage. $K_1 - K_2 V^2 > 0$

Procedure:

- Chose the required relay setting (% of 110V) and TSM
- By the Autotransformer set the circuit to a particular PSM with DPDT at 1
- Put the DPDT to 2 to reset the Relay (disc should return to its original position)
- Switch over to 1 (DPDT), record the time of operation of the Relay, till the contactor trips.
- Repeat 1-4 for at least two TSMs and two relay settings.

Precaution:

- Slowly increase the Voltage to the required value.

Results:

We have successfully studied the working of over voltage relay.

EXPERIMENT NO. - 7



AIM: - Determine the ABCD, H, Z and Image parameters of Short Transmission Line.

Requirements:-

1. Connecting Leads.

Theory:

The transmission lines which have length less than 80 km are generally referred as **short Transmission lines**. For short length, the shunt capacitance of this type of line is neglected and other parameters like electrical resistance and inductor of these short lines are lumped.

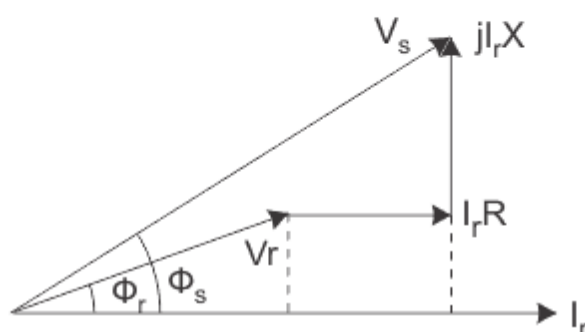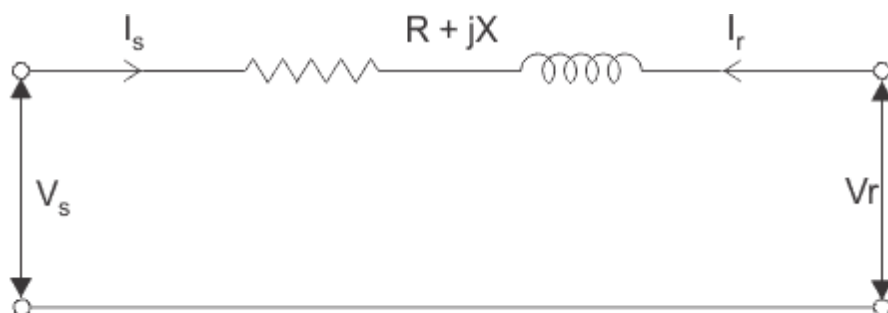**1. Open Circuit the Output Terminal****Procedure:**

- The AC supply is off and variac knob is at zero position
- Make the connection according to the diagram.

- Measure the sending end receiving end current and voltage respectively with the help of switch S1,S2,S3
 - S1 Switch:** Simultaneously get sending end and receiving end voltage, current, active, Reactive, apparent power and power factor.
 - S2 Switch:** get sending end and receiving end active, reactive, apparent power.
 - S3 Switch:** get sending end and receiving end voltage, current, and power factor.
- Select the switch as you want.
- After completion of the entire connection, connect the main cord to the panel & switch on the power supply.
- With the help of variac adjust the voltage up to 110 volt.
- Now by using the values of V_s , I_s & V_r we can easily calculate the dimensionless coefficient A and admittance C.
- Switch off the power system

Dimensionless Coefficient (A) = V_s/V_r

Admittance C = I_s/V_r

2. Short Circuit the Output Terminal

Procedure:

- Short line connection remains same, you have to just short output terminal.
- Measure the sending end receiving end current and voltage respectively with the help of Switch S1, S2, and S3.
 - S1 Switch:** Simultaneously get sending end and receiving end voltage, current, active, reactive, apparent power and power factor.
 - S2 Switch:** get sending end and receiving end active, reactive, apparent power.
 - S3 Switch:** get sending end and receiving end voltage, current, and power factor.
- Select the switch as you want.
- After completion of the entire connection, connect the main cord to the panel & switch on the power supply.

- With the help of variac adjust the voltage up to 110 volt.
- In short test you will get V_s , I_s , I_r values and the values of V_r is zero because output terminal is short circuited.
- By using their values easily find short transmission line Impedance B and Dimensionless Coefficient D.
- Switch off the power supply.

Impedance (B) = V_s/I_r

Dimensionless Coefficient (D) = I_s/I_r

Image Parameter of short line

1. When short line's output terminal was short circuited the ratio of sending end voltage and current is called Z_{sc} .

$$Z_{sc} = V_s/I_s$$

2. When short line's output terminal was open circuited the ratio of sending end voltage and Current is called Z_{oc} .

$$Z_{oc} = V_s/I_s$$

3. Characteristic Impedance (Z_o) = $Z_{sc} * Z_{oc}$

H parameter

$$H_{11} = B/D$$

$$H_{12} = (AD-BC) / D$$

$$H_{21} = -1/D$$

$$H_{22} = C/D$$

Z Parameter

$$Z_{11} = B/C$$

$$Z_{12} = (AD - BC)/C$$

$$Z_{21} = 1/C$$

$$Z_{22} = D/C$$

Results:-

We have successfully studied about the H, Z, and ABCD parameters of short transmission line.

EXPERIMENT NO. - 8


AIM: - Determine the ABCD, H, Z and Image parameters of Medium Transmission Line.

Requirements:

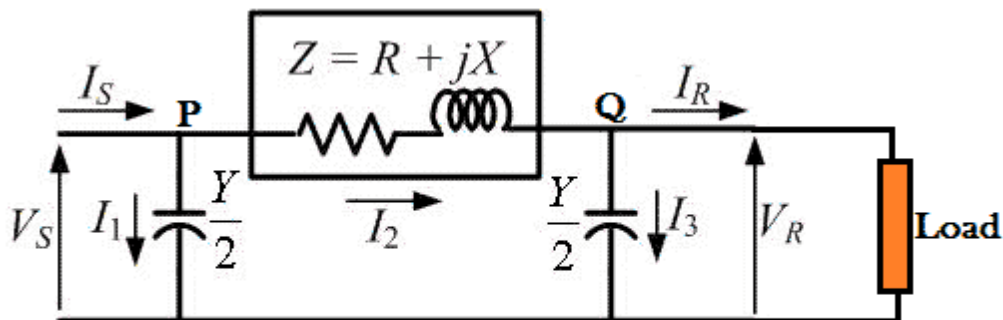1. Connecting Leads

Theory:

The transmission line having its effective length more than 80 km but less than 250 km, is Generally referred to as a **medium transmission line**. Due to the line length being considerably high, admittance Y of the network does play a role in calculating the effective circuit parameters, unlike in the case of short transmission lines. For this reason the modelling of a **medium length transmission line** is done using lumped shunt admittance along with the lumped impedance in series to the circuit.



Nominal π network of medium transmission line.

1. Open Circuit the Output Terminal

Procedure:

- The AC supply is off and variac knob is at zero position
- Make the connection according to the diagram.
- Measure the sending end receiving end current and voltage respectively with the help of switch S1, S2, S3.

S1 Switch: Simultaneously get sending end and receiving end voltage, current, active, reactive, apparent power and power factor.

S2 Switch: get sending end and receiving end active, reactive, apparent power.

S3 Switch: get sending end and receiving end voltage, current, and power factor.

- Select the switch as you want.
- After completion of the entire connection, connect the main cord to the panel & switch on the power supply.
- With the help of variac adjust the voltage up to 220 volt.
- Now by using the values of V_s , I_s & V_r we can easily calculate the dimensionless coefficient A and admittance C.
- Switch off the power system.

Dimensionless Coefficient (A) = V_s/V_r

Admittance C = I_s/V_r

2.Short Circuit the Output Terminal

Procedure:

- Short line connection remains same, you have to just short output terminal.
- Measure the sending end receiving end current and voltage respectively with the help of switch S1, S2, S3.

S1 Switch: Simultaneously get sending end and receiving end voltage, current, active, reactive, apparent power and power factor.

S2 Switch: get sending end and receiving end active, reactive, apparent power.

S3 Switch: get sending end and receiving end voltage, current, and power factor.

- Select the switch as you want.
- After completion of the entire connection, connect the main cord to the panel & switch on the power supply.
- With the help of variac adjust the voltage up to 220 volt.
- In short test you will get V_s , I_s , I_r values and the values of V_r is zero because output terminal is short circuited.

- By using their values easily find short transmission line Impedance B and Dimensionless Coefficient D.
- Switch off the power supply.

Impedance (B) = V_s/I_r

Dimensionless Coefficient (D) = I_s/I_r

Image Parameter of short line

- When short line's output terminal was short circuited the ratio of sending end voltage and current is called Z_{sc} .

$$Z_{sc} = V_s/I_s$$

- When short line's output terminal was open circuited the ratio of sending end voltage and current is called Z_{oc} .

$$Z_{oc} = V_s/I_s$$

- Characteristic Impedance (Z_o) = $Z_{sc} * Z_{oc}$

H parameter

$$H_{11} = B/D$$

$$H_{12} = (AD-BC) / D$$

$$H_{21} = -1/D$$

$$H_{22} = C/D.$$

Z Parameter

$$Z_{11} = B/C$$

$$Z_{12} = (AD - BC)/C$$

$$Z_{21} = 1/C$$

$$Z_{22} = D/C$$

Results:

We have successfully studied about the H, Z, and ABCD parameters of medium transmission line.

EXPERIMENT NO. - 9


AIM:-Determine the ABCD, H, Z and Image parameters of Long Transmission Line.

Requirements:

- Connecting Leads

Theory:

A power transmission line with its effective length of around 250 Kms or above is referred to as a **long transmission line**. Calculations related to circuit parameters (ABCD parameters) of such a power transmission is not that simple, as was the case for a short transmission line or medium transmission line. The reason being that, the effective circuit length in this case is much higher than what it was for the former models.

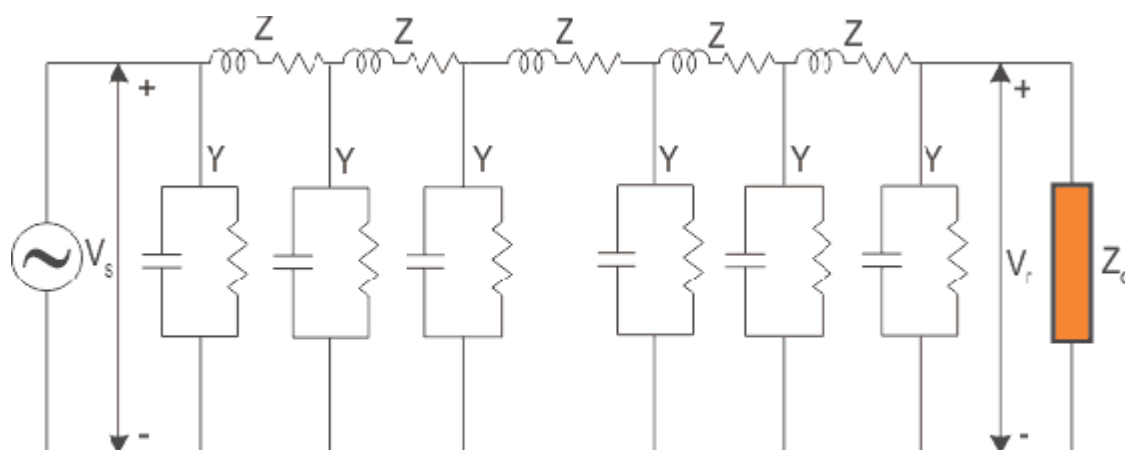

Long Transmission Line Model

1. Open Circuit the Output Terminal

Procedure:

- The AC supply is off and variac knob is at zero position
- Make the connection according to the diagram.
- Measure the sending end receiving end current and voltage respectively with the help of switch S1, S2, S3.

S1 Switch: Simultaneously get sending end and receiving end voltage, current, active, Reactive, apparent power and power factor.

S2 Switch: get sending end and receiving end active, reactive, apparent power.

S3 Switch: get sending end and receiving end voltage, current, and power factor.

- Select the switch as you want.
- After completion of the entire connection, connect the main cord to the panel & switch on the power supply.
- With the help of variac adjust the voltage up to 220 volt.
- Now by using the values of V_s , I_s & V_r we can easily calculate the dimensionless coefficient A and admittance C .
- Switch off the power system.

Dimensionless Coefficient (A) = V_s/V_r

Admittance C = I_s/V_r

2. Short Circuit the Output Terminal

Procedure:

- Short line connection remains same, you have to just short output terminal.
- Measure the sending end receiving end current and voltage respectively with the help of switch S_1 , S_2 , S_3 .

S1 Switch: Simultaneously get sending end and receiving end voltage, current, active, Reactive, apparent power and power factor.

S2 Switch: get sending end and receiving end active, reactive, apparent power.

S3 Switch: get sending end and receiving end voltage, current, and power factor.

- Select the switch as you want.
- After completion of the entire connection, connect the main cord to the panel & switch on the power supply.
- With the help of variac adjust the voltage up to 220 volt.
- In short test you will get V_s , I_s , I_r values and the values of V_r is zero because output terminal is short circuited.

- By using their values easily find short transmission line Impedance B and Dimensionless Coefficient D.
- Switch off the power supply.

Impedance (B) = V_s/I_r

Dimensionless Coefficient (D) = I_s/I_r

Image Parameter of short line

When short line's output terminal was short circuited the ratio of sending end voltage and Current is called Z_{sc} .

$$Z_{sc} = V_s/I_s$$

When short line's output terminal was open circuited the ratio of sending end voltage and Current is called Z_{oc} .

$$Z_{oc} = V_s/I_s$$

$$\text{Characteristic Impedance } (Z_o) = Z_{sc} * Z_{oc}$$

H parameter

$$H_{11} = B/D$$

$$H_{12} = (AD-BC) / D$$

$$H_{21} = -1/D$$

$$H_{22} = C/D$$

Z Parameter

$$Z_{11} = B/C$$

$$Z_{12} = (AD - BC)/C$$

$$Z_{21} = 1/C$$

$$Z_{22} = D/C$$

Results:

We have successfully studied about the H, Z, and ABCD parameters of long transmission line.

EXPERIMENT NO. - 10

AIM: - Study of Flash & Fire Point test of Transformer oil.

Requirements:

1. Transformer Oil
2. Electric Lighter

Theory:

Transformer oil or **insulating oil** is a highly refined mineral oil that is stable at high Temperatures and has excellent electrical insulating properties. It is used in oil filled Transformers, some types of high voltage capacitors, fluorescent lamp ballasts, and some Types of high voltage switches and circuit breakers. Its functions are to insulate, Suppress corona and arcing, and to serve as a coolant.

Procedure:

- Ensure that mains switch at the control set-up is at off position
- Clean oil cup carefully to avoid any contamination and fill half a cup from transformer oil
- Keep the oil cup into its respective position
- Adjust the thermostat rod in such a way that it must be half filled into oil cup and tighten it by providing screw on its stand.
- Cover up oil cup.
- Switch on mains as well as the MCB
- Observe the temperature start increasing from its normal temperature.
- Now observe the oil until it evaporates and vapors comes out from the oil cup.
- Now use electric lighter to ignite the oil by uncover half of the oil cup.
- Times when oil catch fire for a large time indicates fire point of the oil.
- Cover up the oil cup to extinguish fire into oil cup.

- Push heating on/off switch to stop heating indicated by red LED blow out.
- Switch off mains as well as the MCB.

Results:

Flash Point of the Transformer oil: -140°C